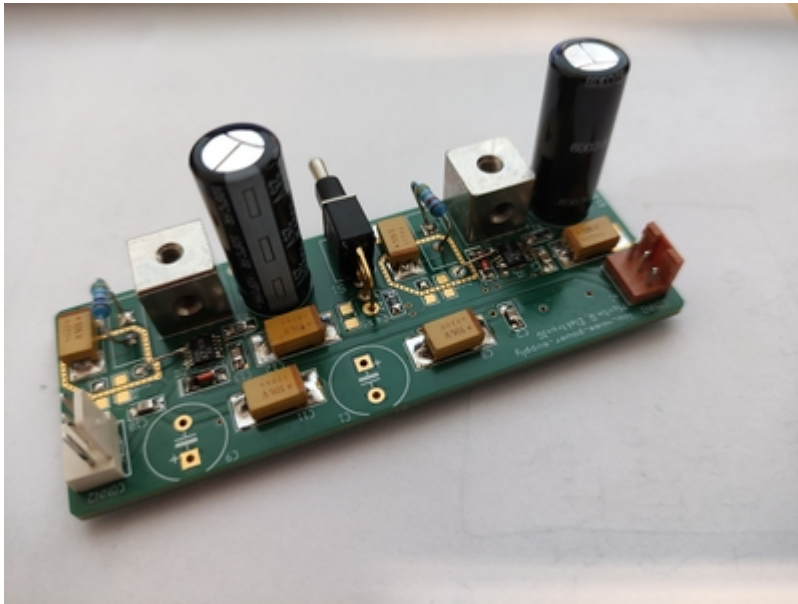


Low noise power supply



Function

- This PCB is a power supply board based on the ICs LT3045 and LT3094, that are low-noise voltage controller, i.e. low-noise alternatives to the commonly used 7815 and 7915 parts. Output voltages are set by a resistor, up to +15 and -19 V.

Options

- The output voltages can be set via a resistor.
- The supply can be turned on or off via a switch, but you could also solder a TTL signal to it.

Performance

- Noise performance has not been tested yet!

Date

- Schematic and PCB was drawn August 2021

Status

- Not implemented yet. Not tested yet.

Author

Martin Quensen, quensen@iqo.uni-hannover.de

Schaltungsprinzip


- It's best to read the datasheet for the LT3045 to understand what was done here. The LT3094 is essentially the negative version of it, with no additional features.
- The turning on/off function was implemented using a mechanical switch.
- The current limiting function was implemented by a fixed SMD resistor.
- Thermal considerations were considered by placing the parts close to an solid metal block that is supposed to be fixed to the casing.

Schematics and layout

- [Git](#)
- [Layout png](#)
- Schematic 2021-08-03

Meckerliste

What need to be improved: (

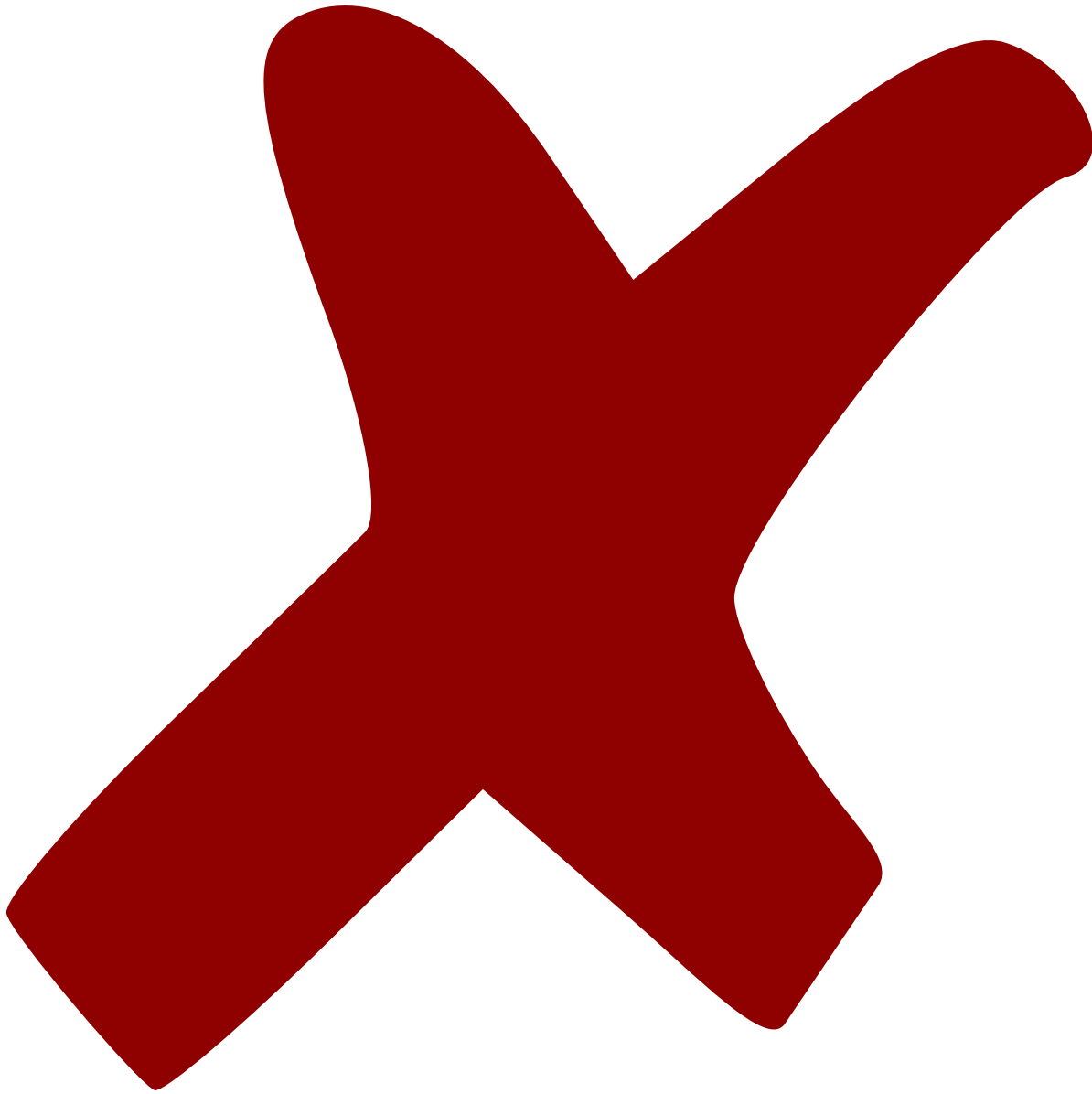







)

From:
<https://elektroniq.iqo.uni-hannover.de/> - **ElektronIQ**

Permanent link:
https://elektroniq.iqo.uni-hannover.de/doku.php?id=eigenbau:supplies:low_noise_power_supply:start&rev=1640004991

Last update: **2021/12/20 12:56**

